

Date	/	/
Page No.		

Electrical

Engineering

Kavya Dixit


BTBT C23147

Submitted to - Vivek Sir



Date	1 / 1
Page No.	1

4.4.2

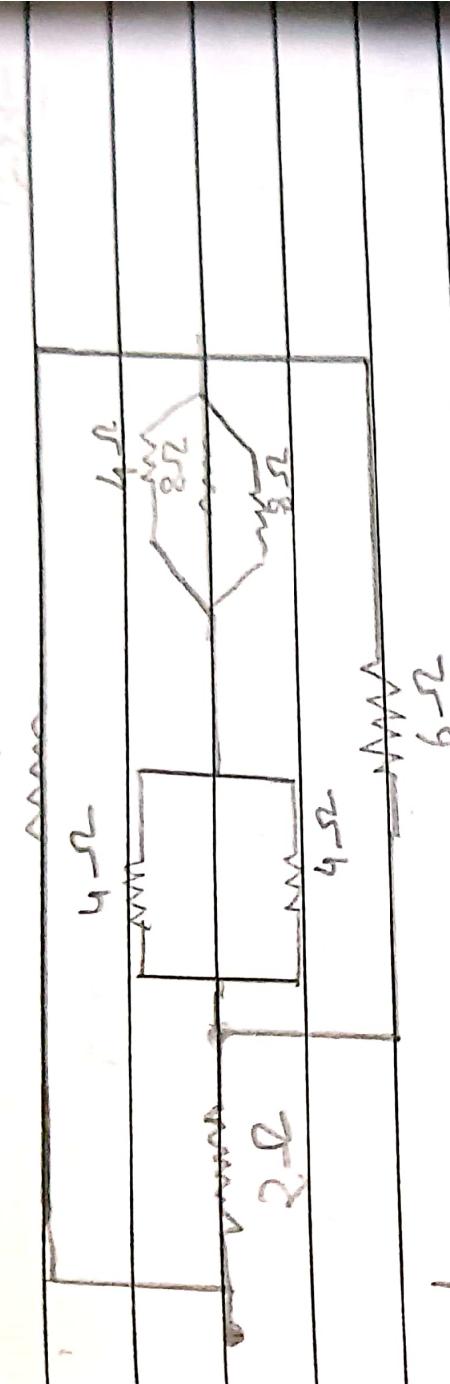


Ans. $\frac{U_o}{U_i} = \frac{2R}{2R + 2\Omega}$

$$U_o = U_i \cdot \frac{2R}{2R + 2\Omega}$$

(a)
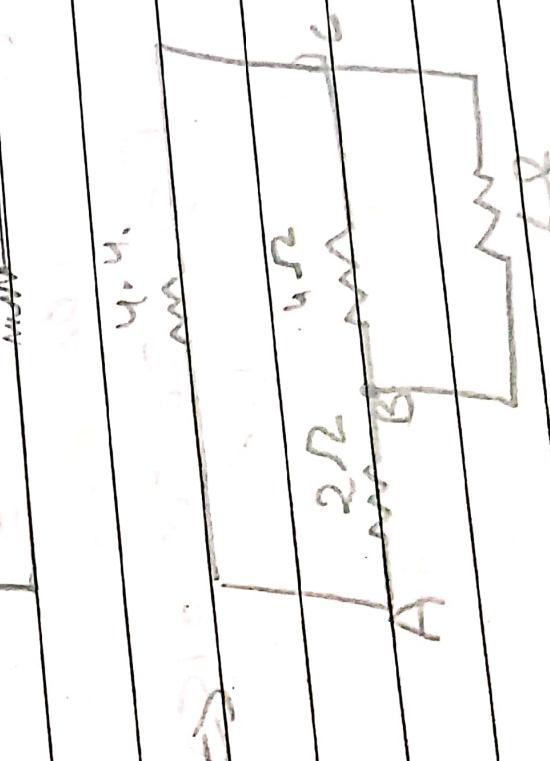
$$U_o = 4.5 \cdot \frac{2 \cdot 6.5}{2 \cdot 6.5 + 2} = 4.5 \cdot \frac{13}{14} = 4.42857 \text{ V}$$




Ans. $\frac{U_o}{U_i} = \frac{2R}{2R + 2\Omega}$

$$U_o = 2.5 \cdot \frac{2 \cdot 6.5}{2 \cdot 6.5 + 2} = 2.5 \cdot \frac{13}{14} = 2.42857 \text{ V}$$

(b)



Scanned with OKEN Scanner

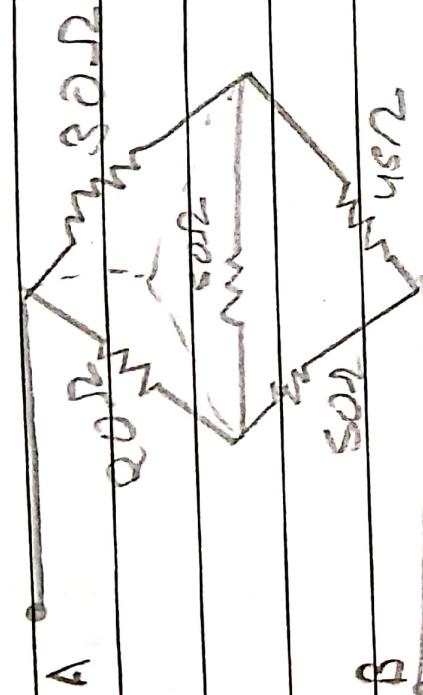


By star delta transformation


$$R_{12} = \frac{20 \times 50}{(20+50+30)} = 10\Omega$$

$$R_{23} = \frac{20 \times 30}{100} = 6\Omega$$
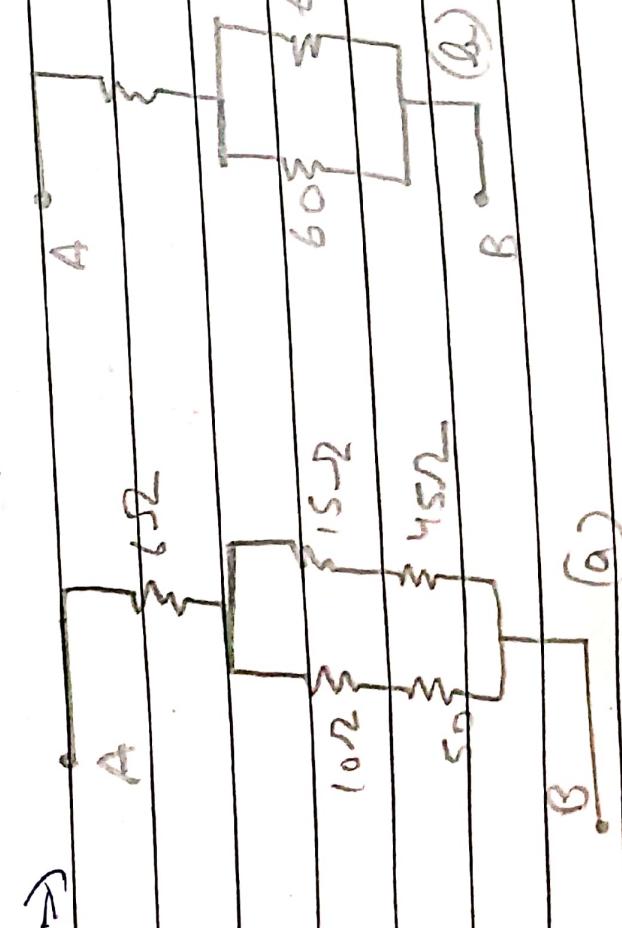
$$R_{31} = \frac{50 \times 30}{100} = 15\Omega$$




c) $A = \frac{1}{6}$ for fig (a)

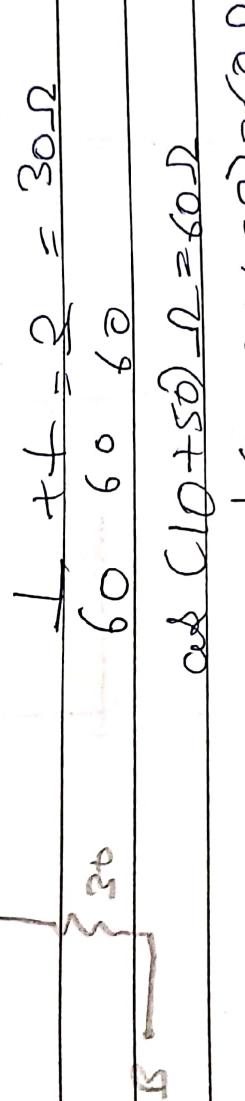


and $(15\Omega + 45\Omega) = 60\Omega$
 $(6 + 30)\Omega = 36\Omega = R_{AB}$ for A & B

Ans 3

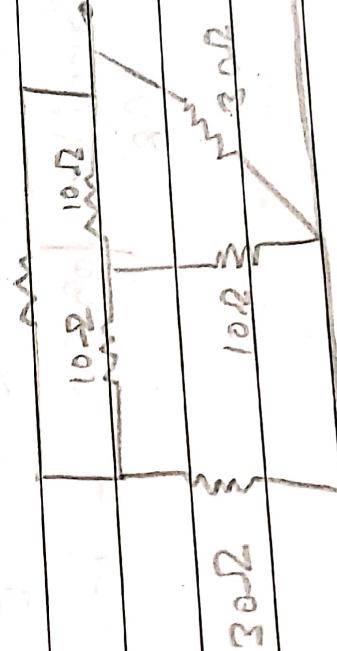

Ans

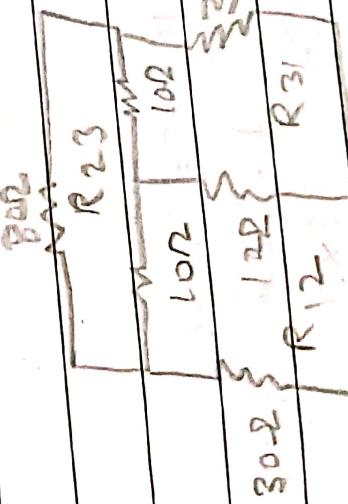

By star delta transformation

$$R_{AB} = R_1 + R_2 + R_3 = 10 + 10 + 10 = 30\Omega$$




By formula,
 $R_{AB} = R_A + R_B + R_C$

$$R_{12} = R_{23} = R_3 = 30\Omega$$

Date / /
Page No.

Nov, 2

30

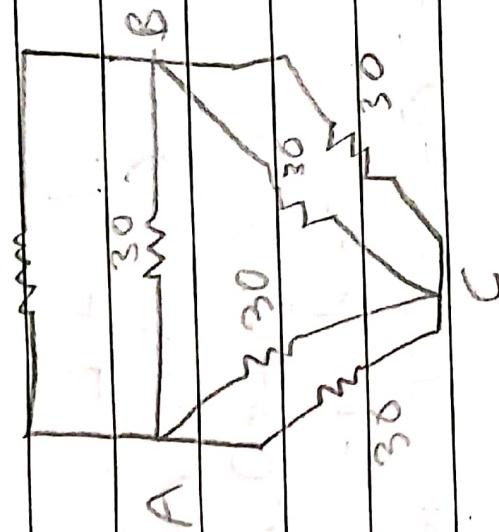


$$\text{Incase value } AC \Rightarrow \frac{1}{30} + \frac{1}{30} = \frac{2}{30} = \frac{1}{15}$$

L2 Similar for BC = 150

AB

C

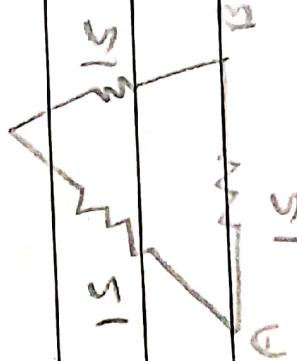


$$15 + 15 = 30 \text{ D.}$$

$$\text{L2 } \frac{1}{30} + \frac{1}{15} = \frac{2}{30} = \frac{1}{15} \text{ D.}$$

Date	1/1/1
Page No.	1

9.2

9.2

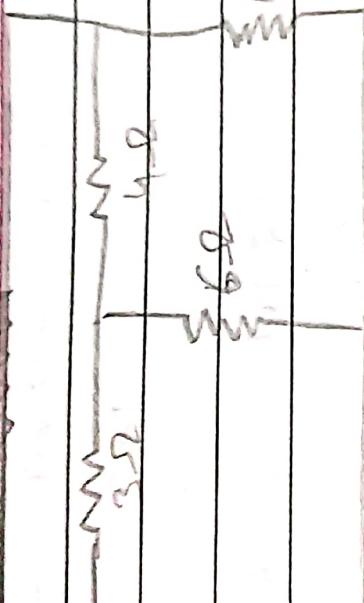


B

By Star delta transformation

$$R_{12} = 6 + 3 + \frac{6 \times 3}{6} = 13.5$$

$$R_{23} = \frac{3 + 4 + \frac{3 \times 4}{3}}{6} = 9$$
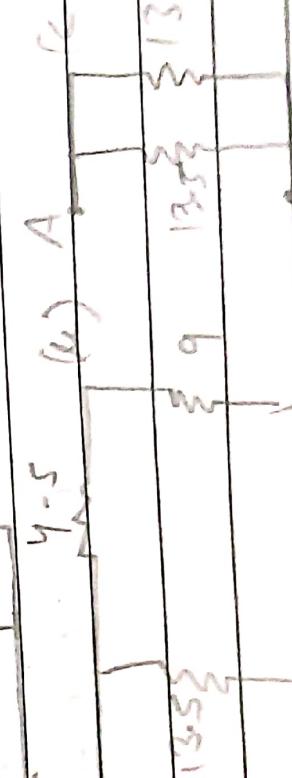
$$R_{31} = 6 + 4 + \frac{6 \times 4}{3} = 18$$



$$B = \frac{9 \times 13.5}{9 + 13.5 + 18}$$

$$a \rightarrow (9 \parallel 9) = \frac{9 \times 9}{9+9} = 4.5$$

$$\underline{18 \times 18} + \underline{z 18 \Omega}$$

$$18+18$$


ie) $4.5 + 9 = 13.5$

c) $\underline{13.5 \times 13.5} \Rightarrow 6.75 \Omega$

$$13.5 + 13.5$$

6Ω

Ans




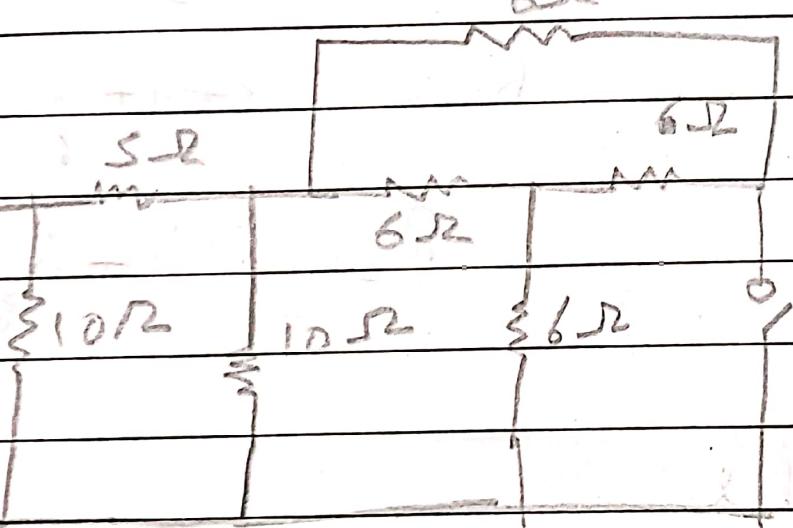


Switch is closed


By Star delta transformation

$$R_{1Q} \rightarrow 6+6 + 6 \times 6 = 18 = R_{23} = R_{31}$$


$\cancel{6}$

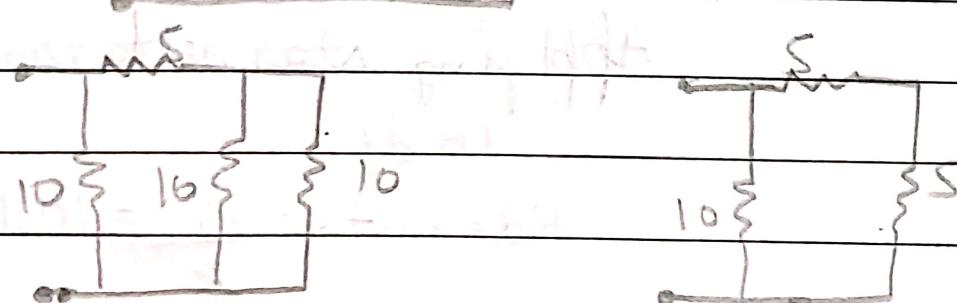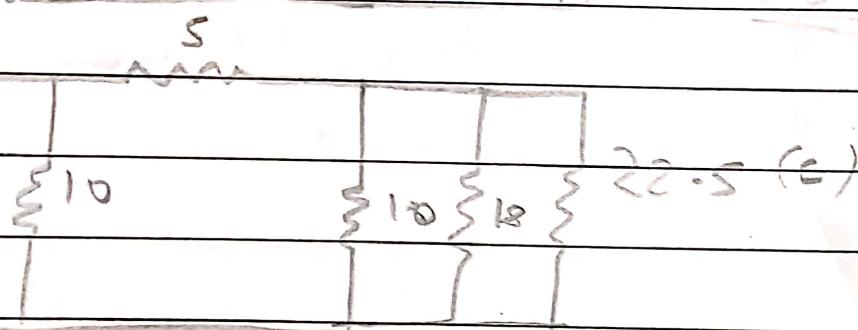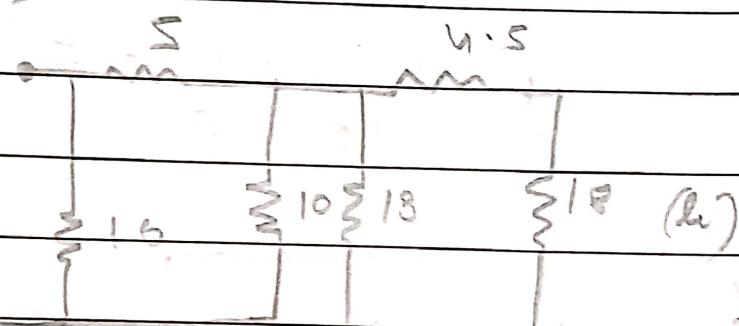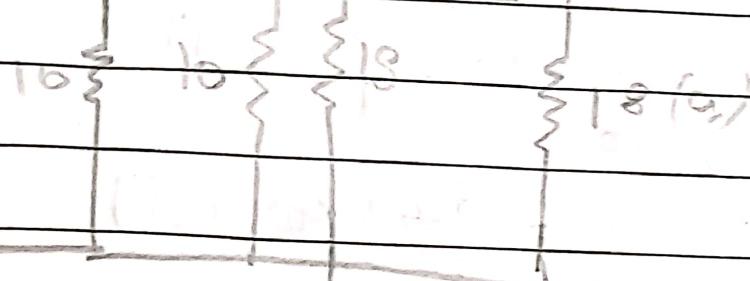SD \rightarrow 6.52

(d)

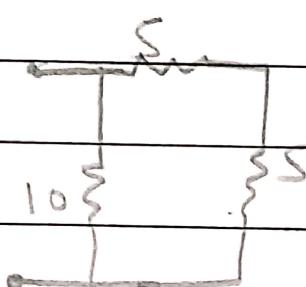

(e)

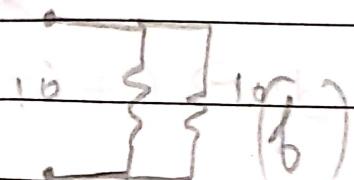

$$\text{fig (a)} \rightarrow \frac{1}{6} + \frac{1}{18}$$

$$= 4.552$$

$$\text{Q) } 4\Omega + 8 = 22\Omega \text{ (series)}$$


$$\text{C) } \frac{1}{22\Omega} + \frac{1}{18} = 10\Omega \text{ (parallel)}$$

$$\text{D) } \frac{1}{10} + \frac{1}{10} = 5\Omega \text{ (parallel)}$$

$$\text{E) } 5 + 5 = 10\Omega \text{ (series)}$$

$$\text{F) } \frac{1}{10} + \frac{1}{10} = 5\Omega \text{ (parallel)}$$

Ans-6

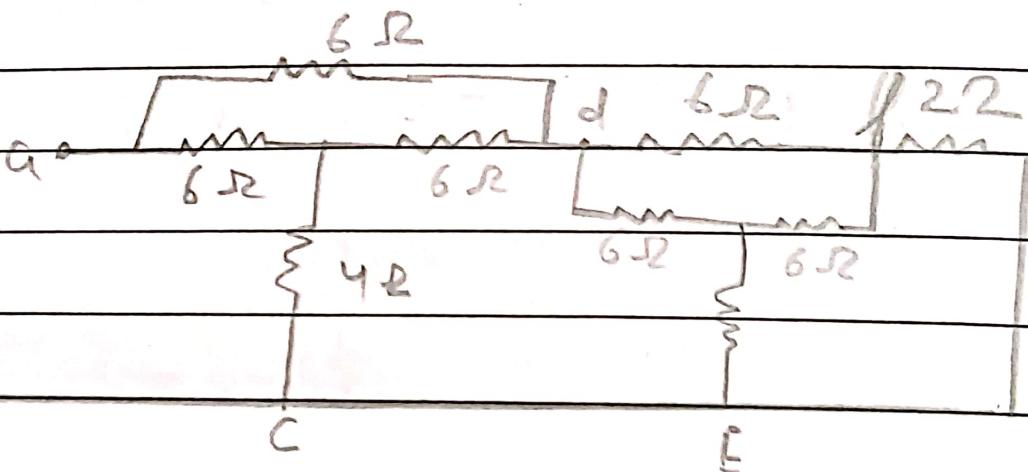

Applying star delta transformation
In dfc.

$$R_{de} \rightarrow 6 + 2 + \frac{6 \times 2}{6} = 10\Omega$$




$$R_{fc} \rightarrow 6 + 2 + \frac{6 \times 2}{6} = 10\Omega$$


$$R_{df} \rightarrow 6 + 6 + \frac{6 \times 6}{6} = 30\Omega$$

Applying star delta in a/c,


$$R_{ad} \rightarrow 6 + 6 + \frac{6 \times 6}{4} = 21.2$$
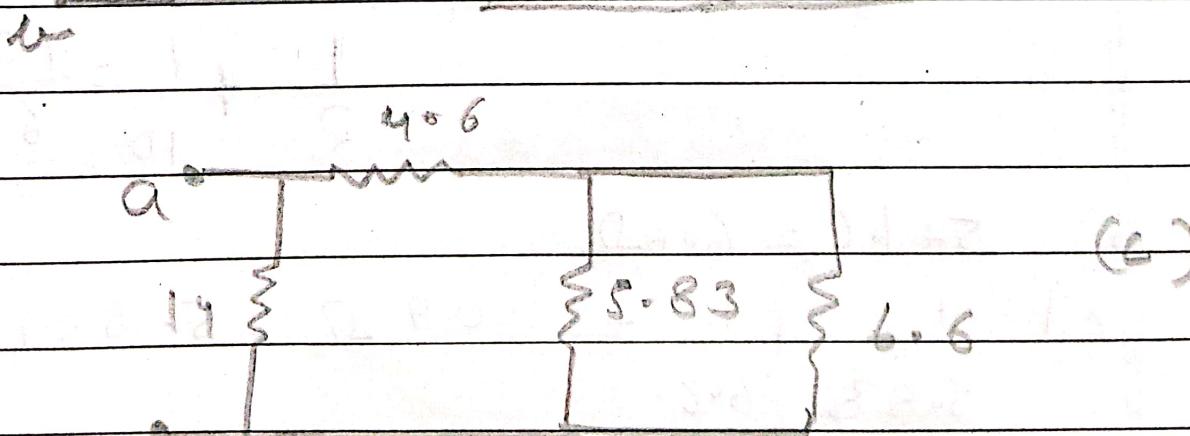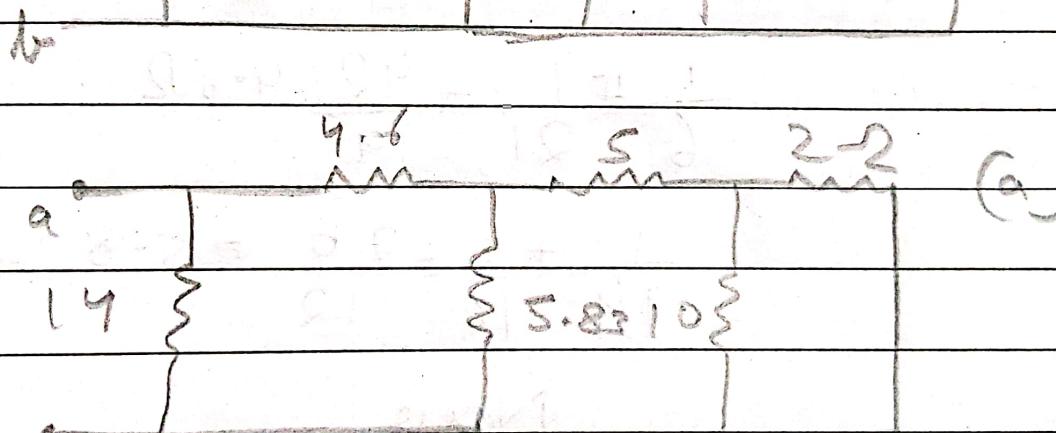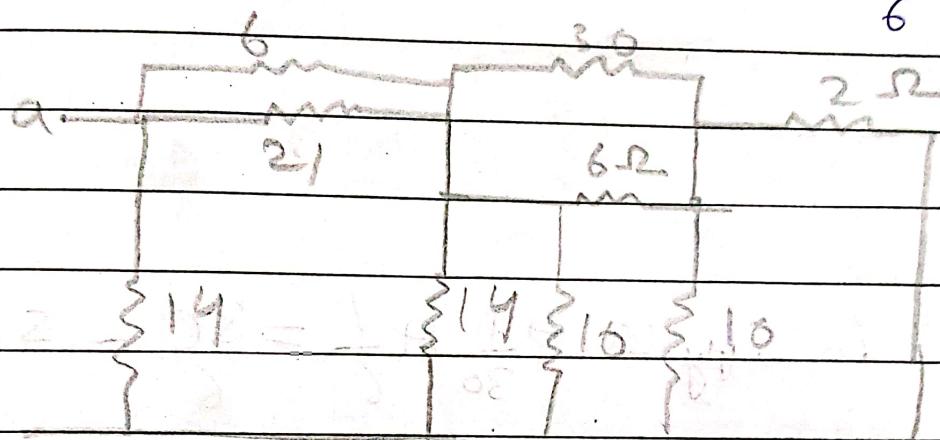
$$R_{ac} \rightarrow 6 + 4 + \frac{6 \times 4}{6} = 14.2 = R_d$$



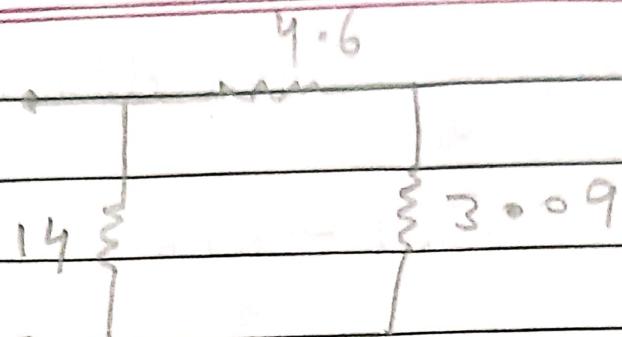

(a)

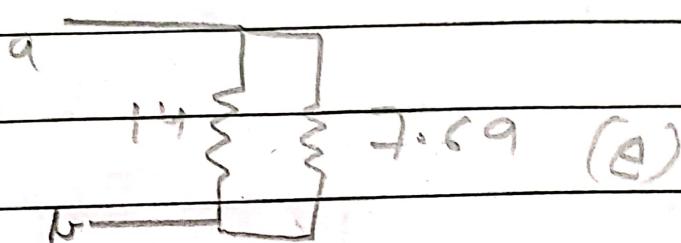

(e)

$$\text{in fig (a)} \Rightarrow \frac{1}{30} + \frac{1}{6} = \frac{30}{6} = 5.0$$

$$\frac{1}{6} + \frac{1}{21} = \frac{42}{9} = 4.62$$

$$\frac{1}{14} + \frac{1}{10} = \frac{20}{12} = 5.832$$

Now,

$$\frac{1}{2} + \frac{1}{10} = \frac{10}{6} = 1.62$$

$$) \quad 5 + 1.6 = 6.62$$


$$c) \quad \frac{1}{5.83} + \frac{1}{6.6} = 3.09 \quad (5.83 \times 6.6)$$

$$) \quad 4.6 + 3.09 = 7.69 \quad (4.6 - 3.04)$$

$$\text{e) } \frac{14 \times 7.69}{14 + 7.69} = 4.96 \approx 5.2$$

(14117.69)

Avg

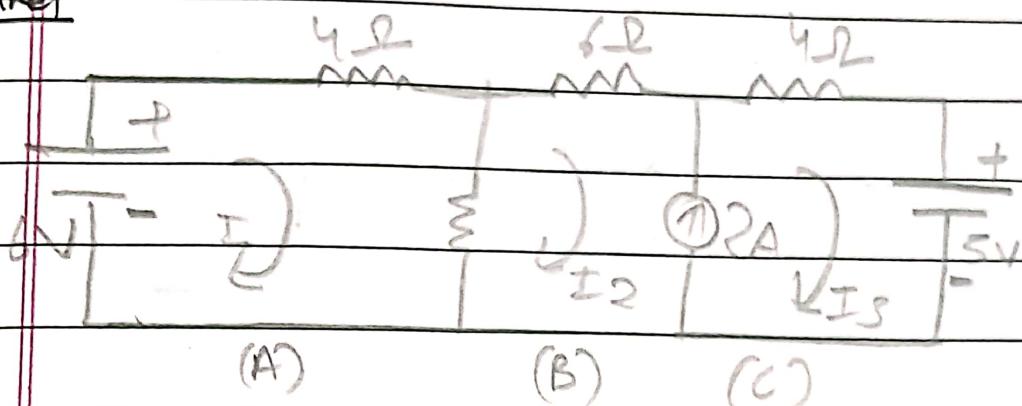

$$\text{In mesh A} \rightarrow -4I_1 - 5(I_1 - I_2) + 6 = 0$$

$$\text{mesh B} \rightarrow -6I_2 - 5(I_2 - I_1) = 0$$

$$\text{mesh C} \rightarrow -4I_3 - 5V = 0$$

$$= 6I_2 - 5I_2 + 5I_1 = 0$$

$$7I_1 - 5I_2 = 0 \quad I_2 = \frac{7}{5}I_1$$

~~$$\text{In mesh A} \rightarrow -4I_1 - 5I_1 + 5I_2 + 6 = 0$$~~

~~$$-9I_1 + 5I_2 + 6 = 0$$~~

~~$$-9I_1 + 2 \cdot 2.5I_2 + 6 = 0$$~~


~~$$6.75I_1 + 6 = 0$$~~

$$I_1 = \frac{-6}{6.75} \quad I_1 = -0.88$$

$$0.45 \times 0.88 = I_2 \quad \therefore I_2 = -0.39$$

current through
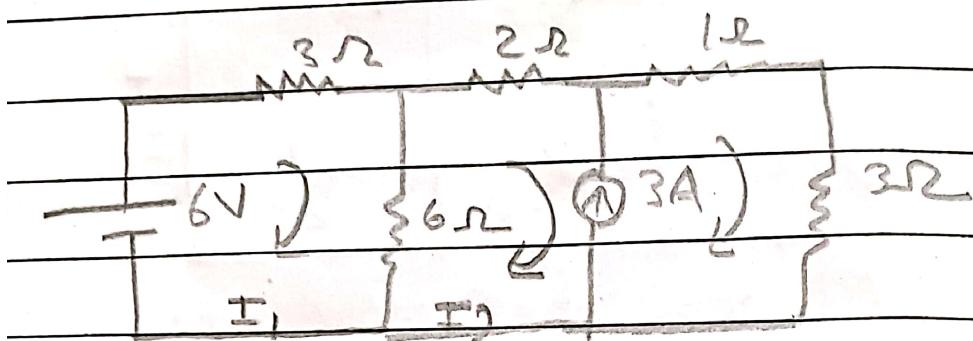
$$I_2 \rightarrow \frac{(0.75 - (-0.39))}{-11.14}$$



$$(A) = (B) = +1.5A$$

$$I_2 = 3A > I_3$$

$$\text{for Mesh 1} \rightarrow -3I_1 - 6(I_1 - I_2) + 6 = 0$$

$$-3I_1 - 6I_1 + 6I_2 + 6 = 0$$

$$-9I_1 + 6I_2 + 6 = 0$$

$$6 = 9I_1 - 6I_2 \quad \boxed{-\textcircled{1}}$$

mesh 2 →

$$-6(I_2 - I_1) - 2I_2 = 0$$

$$-6I_2 + 6I_1 - 2I_2 = 0 \quad 6I_1 = 8I_2$$

$$I_1 = \frac{4}{3}I_2$$

$$6 = 9 \left(\frac{4}{3}I_2 \right) - 6I_2$$

$$6 = I^2 I_2 - 6I_2$$

$$6 = 6I_2$$


$$\therefore I_2 = 1$$

$$1 + 3 = I_3$$

$$\therefore I_3 = 4A$$

Now,
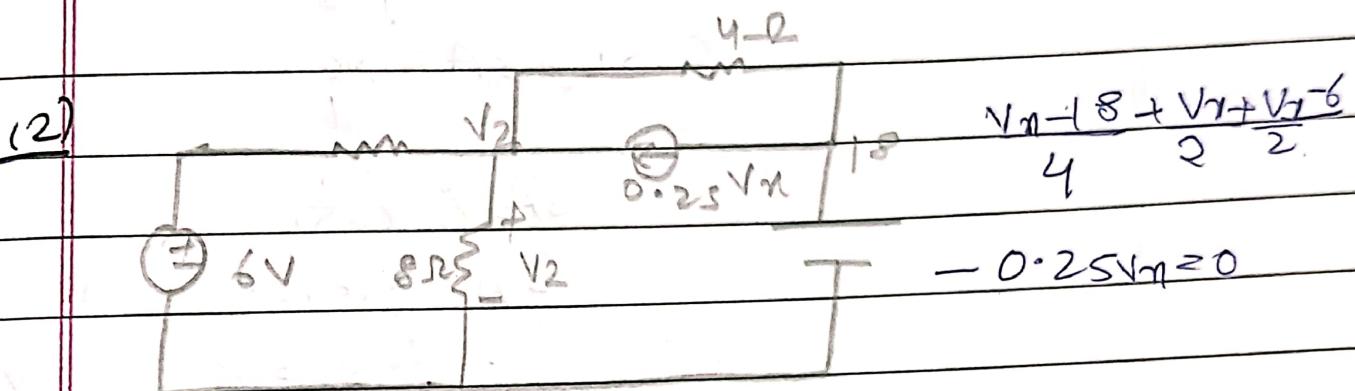
$$I_2 = 4 - \left(\frac{4 \times 3}{4} \right) \therefore 4 - 3 = 1A \quad (\text{Ans})$$



$$\frac{V_R1 - 18}{4} = -\frac{V_R1 + 6}{2} - \frac{V_R2}{2} + 0.25V_R3$$

$$\frac{V_R1 - 18}{2X} = -\frac{V_R1 + 6}{2} - V_R2 + 0.5V_R3$$

$$\frac{V_R1 - 18}{2} = -2V_R2 + 0.5V_R3 + 6$$

$$\frac{V_R1 - 18}{2} = -1.5V_R2 + 6$$

$$V_R1 - 18 = -1.5V_R2 + 1$$

$$V_R1 - 18 = -3V_R2 + 12$$


$$4V_R2 = 30$$

$$V_R2 = 7.5V$$

$$V_x + V_2 - 18 = -1.5 V_x + 6$$

$$V_x - 18 = -3 V_x + 12$$
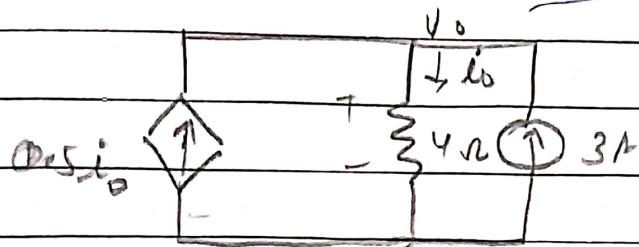
$$4 V_x = 30 \quad \therefore V_x = 7.5 \text{ V}$$



$$i_o = \frac{V_o - 0}{4}$$


now, incoming currents = outgoing current

$$0.5 i_o + 3A = V_o = i_o$$

$$3A = i_o - 0.5 i_o$$

$$3A = 0.5 i_o \quad \therefore i_o = 6A$$

$$\therefore V_o = 6 \times 4 = 24V.$$

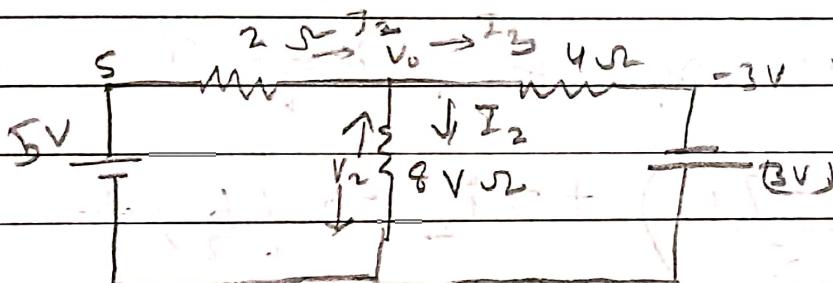

$$\text{By fig.} \rightarrow I_1 = I_2 + I_3$$

$$5 - V_o = V_o - 0 + \frac{2 V_o + 6 V}{8}$$

$$\frac{5 - V_o}{2} = \frac{V_o - 0}{8} + \left(\frac{2 V_o + 6 V}{8} \right)$$

$$\frac{5 - V_o}{2} = V_o + 2 V_o + 6$$

$$4(5 - V_o) = 3 V_o + 6 \Rightarrow 20 - 4 V_o = 3 V_o + 6$$


$$14 = 7 V_o \quad \boxed{V_o = 2}$$

$$I_1 = \frac{5 - 2}{2} = \frac{3}{2} = 1.5 \text{ A}, \quad V_1 = 1.5 \times 2 = 3 \text{ V.}$$

$$I_2 = \frac{2}{4} = \frac{1}{2} = 0.25 \text{ A}, \quad V_2 = 8 \times 0.25 = 2 \text{ V.}$$

$$I_3 = \frac{2}{4} + \frac{3}{4} = \frac{5}{4} = 1.25 \text{ A}, \quad V_3 = 4 \times 1.25 = 5 \text{ V.}$$

Ans 17:

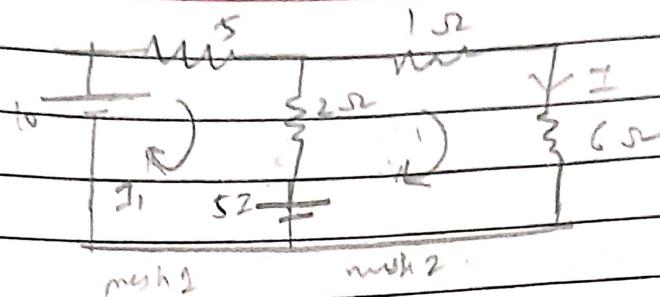

for mesh 1.

$$10 - 5(I_1) - 2(I_1 - I_2) - 5I = 0$$

$$10 - 7I_1 + 2I_2 - 5I = 0$$

$$\text{mesh 2} \rightarrow -1i_2 - 6i_2 + 5i - 2(I_2 - I_1) = 0$$

$$-9i_2 + 2i_1 + 5I = 0 \quad \text{(2)}$$

Adding eqn (1) & (2)

$$10 - 7i_1 + 2i_2 - 5I - 9i_2 + 2i_1 + 5I = 0$$

$$10 - 5i_1 - 7i_2 = 0$$

$$\Rightarrow \boxed{\frac{10 - 7i_2}{5} = i_1} \quad \text{now } \boxed{I_2 = I_1 \times \frac{6}{7}}$$

Putting value of I_1 & I_2 in eqn (1)

$$10 - 7\left(\frac{10 - 7i_2}{5}\right) + 2i_2 - 5\left(\frac{6}{7}\right)i_2 = 0$$

$$35(10) - 7(70 - 49i_2) + 7i_2 - 150i_2 = 0$$

$$350 - 490 + 343i_2 + 7i_2 - 150i_2 = 0$$

$$140 = 263i_2 \quad i_2 = \frac{140}{263} = 0.532$$


$$\Rightarrow 10 - 5i_1 - 7i_2$$

Putting the value of i_2 in this eqn

$$10 - 5i_1 - 7(0.532) = 0$$

$$10 - 5i_1 - 3.71 = 0$$
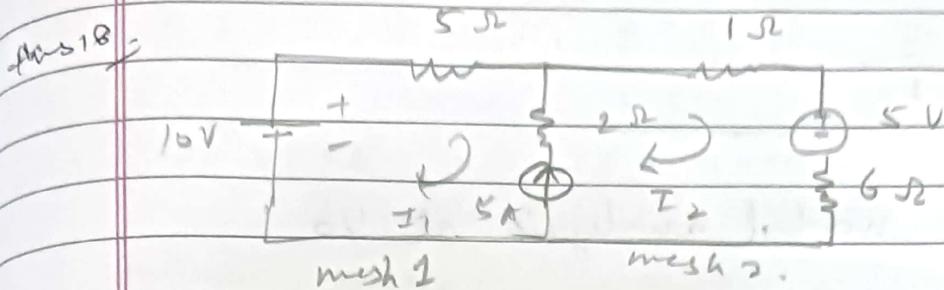
$$-5i_1 = -6.29 \therefore i_1 = 6.29/5 = 1.25$$



→ In mesh 1.

$$10V - 5i_1 + 2(i_1 - i_2) = 0$$

$$10 - 5i_1 - 2i_1 + 2i_2 = 0$$

$$10 - 7i_1 + 2i_2 = 0 \quad \textcircled{1}$$

→ mesh 2

$$i_2 - 5 - 6i_2 - 2(i_2 - i_1) = 0$$

$$i_2 - 5 - 6i_2 - 2i_2 + 2i_1 = 0$$

$$-5 = 7i_2 + 2i_1 = 0$$

$$(5 + 7i_2) = 2(i_1) \Rightarrow \frac{5 + 7i_2}{2} = i_1$$

$$10 - 7\left(\frac{5 + 7i_2}{2}\right) + 2i_2 = 0$$

$$10 - \left(\frac{35 + 49i_2}{2}\right) + 2i_2 = 0$$

$$20 - 35 - 49i_2 + 4i_2 = 0$$

$$-15 - 45i_2 = 0$$


$$-15 = 45i_2$$

$$i_2 = -\frac{1}{3} \therefore i_2 = -0.33$$

$$i_1 = \frac{5 + 7(-0.33)}{2} = 5 - \frac{2.31}{2} = 1.34$$

Now current flows through 1Ω .

Ans 19.

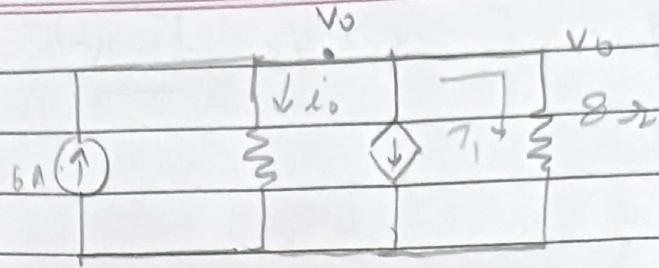applying nodal analysis at V_0

$$6 = i_0 + i_0 \frac{V_0}{4} + i_1 \quad \text{---(1)}$$

$$6 = \frac{4i_0}{4} + i_0 + \frac{V_0}{8} = 5i_0 + \frac{V_0}{8}$$

$$48 = 7i_0 + V_0 \quad \text{---(2) nzo}$$


as in parallel voltage remains same,

∴ V_0 is the potential diff. b/w 2 nodes

$$\therefore i_0 = \frac{V_0}{8}$$

$$48 = 10 \left(\frac{V_0}{8} \right) + V_0 \Rightarrow 48 = 6V_0$$


$$\boxed{V_0 = 8V} \quad \therefore \boxed{i_0 = 4A}$$

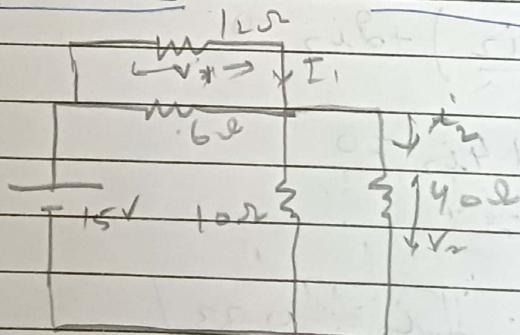Solving 6Ω & 12Ω in parallel

$$\frac{1}{6} + \frac{1}{12} = \frac{12}{3} = 4\Omega$$

Similarly solving 10Ω & 40Ω in parallel
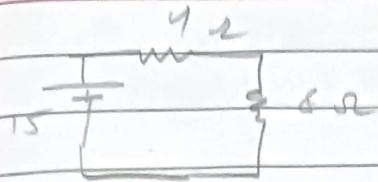
$$\frac{1}{10} + \frac{1}{40} = \frac{40}{3} = 8\Omega$$



Now as 8Ω & 4Ω
are in series.

$$8+4=12\ \Omega$$

$$\therefore V = IR$$

$$15 = x \times 12 \quad \therefore x = I = \frac{15}{12}$$

$$\therefore I = 1.25$$

as current in series remains same.

$$\therefore I_{9\Omega} = I_{8\Omega} = 1.25$$

Now applying current division rule

Rule is 12Ω & 6Ω

$$1.25 \times \frac{8}{12+6} = 1.25 \times 0.33 = 0.41$$

CD.R. (Current division rule)

in 12Ω & 4Ω .

$$1.25 \times \frac{4}{12+4} = 0.25$$


$$\text{Now } V_{12\Omega} = 0.41 \times 12 = 4.92V$$

$$V_{4\Omega} = 0.25 \times 4 = 1.0V$$

$$\text{Now } P_{12} = VI = 0.41 \times 4.92 = 2.012 \text{ W}$$

$$P_{4\Omega} = VI = 1.0 \times 0.25 = 0.25W$$

Ans 2/1

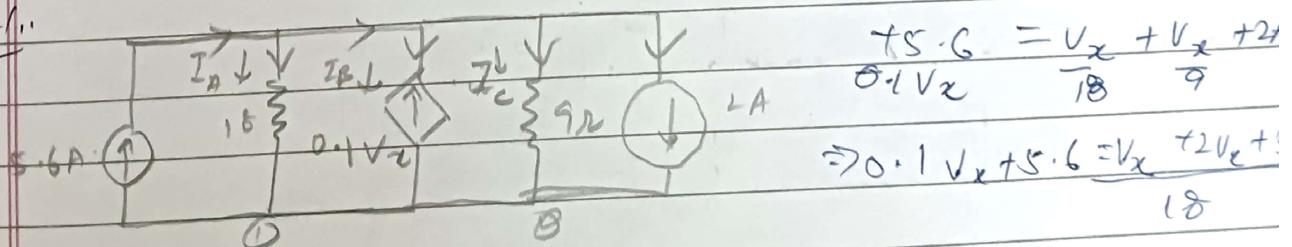

$$(0.1V_x + 5.6)18 = 3V_x + 36$$

$$1.8V_x + 100.8 = 3V_x + 36$$


$$100.8 - 36 = 1.2V_x \Rightarrow 64.8 = 1.2V_x$$

$$64.8 = V_x \therefore [V_x = 54]$$

1.2

$$i_A = \frac{54}{18} = 3A \quad i_B = 0.1 \times 54 = 5.4A$$

$$\dot{i}_{ic} = \frac{54}{9} = 6A$$

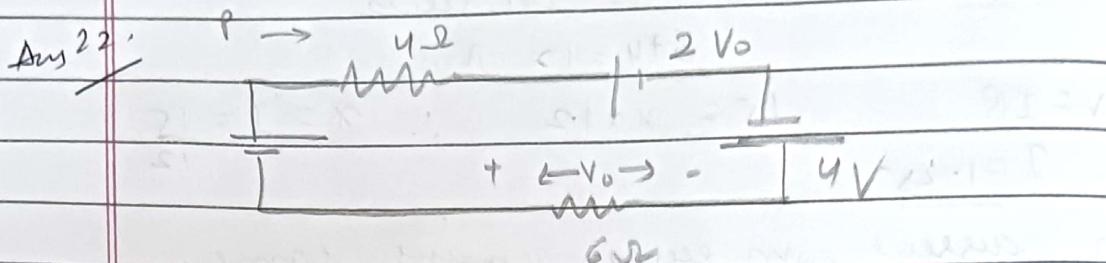

Applying KVL.

$$-4i - 2V_0 + 4V + 12V - 6i = 0$$

$$\text{now as } 6I = V_0 \therefore I = \frac{V_0}{6}$$

$$-10i - 2V_0 + 16V = 0$$



$$-10 \left(\frac{V_0}{6} \right) - 2V_0 = -16$$

$$-1.66V_0 - 2V_0 = -16$$

$$-3.66V_0 = -16 \Rightarrow V_0 = 16$$

$$V_0 = 16V$$
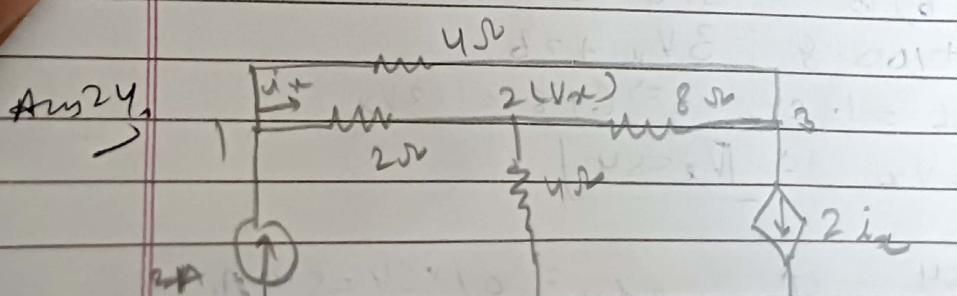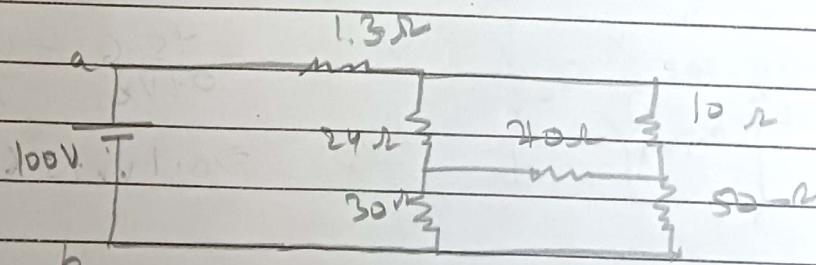
$$\text{Now, } P = \frac{4 \cdot 37}{6} = 0.72A$$



for node 1

$$2 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} \quad \rightarrow \textcircled{1}$$

node 2

$$\frac{V_1 - V_2}{2} + \frac{V_2 - V_3}{4} = \frac{V_2}{4} + \frac{V_2 - V_3}{8} \quad \textcircled{2}$$

node 3

$$\rightarrow \frac{V_2 - V_3}{8} + \frac{V_1 - V_3}{4} = 2 \left(\frac{V_1 - V_2}{2} \right)$$

Solving eqn $\textcircled{1}, \textcircled{2} \& \textcircled{3}$

$$3V_1 - 2V_2 - V_3 = 8 \quad \textcircled{4}$$

$$6V_1 - 7V_2 - V_3 = 0 \quad \textcircled{5}$$

$$9V_2 - 3V_3 - 6V_1 = 0 \quad \textcircled{6}$$

now adding eqn $\textcircled{5} \& \textcircled{6}$

$$9V_2 - 3V_3 - 6V_1 + 6V_1 - 7V_2 - V_3 = 0$$

$$\boxed{V_2 = 2V_3}$$

Subtracting eqn $\textcircled{4}$ from $\textcircled{5}$

$$6V_1 - 7V_2 - V_3 - (3V_1 - 2V_2 - V_3 - 8) = 0$$

$$\boxed{V_2 = \frac{3V_1 + 8}{5}} \rightarrow \text{subs. value of } V_2 \text{ in eqn 6}$$

$$9V_2 - 3\left(\frac{V_1 + 8}{5}\right) - 8\left(\frac{5V_1 - 8}{5}\right) = 0$$


$$15V_2 - (-1 - 3) + 16 = 0$$

$$\boxed{V_2 = 6.4}$$


$$\therefore V_1 = 5\left(\frac{6.4}{3}\right) - 8 = 8$$

$$V_3 = \frac{6.4}{2} = 3.2 \quad \text{now } V_1 = 6.4 - 8 = 1.6 \text{ V}$$

same at $V_3 (1.6)$ (as in 11 voltage remains same)
 at 2 $\rightarrow 8 - 6.4 - 3.2 = 3.2$

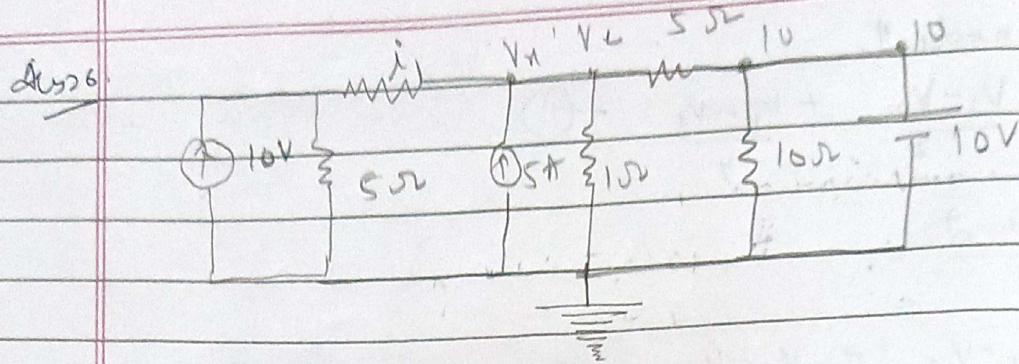

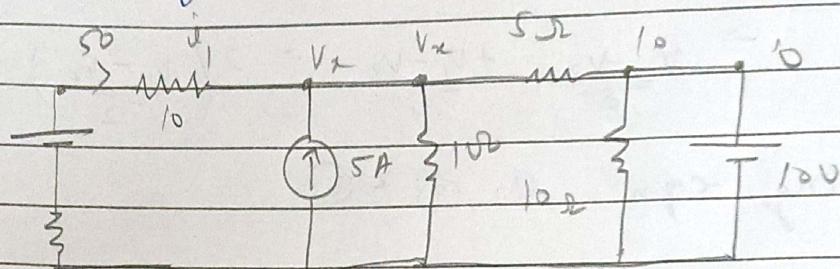Converting 10A. source into voltage source



using KVL across V_x

$$\frac{50 - V_x}{10} + 5 = \frac{V_x}{2} + \frac{V_x - 10}{5}$$


$$\frac{50 - V_x + 50}{10} = \frac{5V_x + V_x - 10}{5}$$

$$100 - V_x = 12V_x - 20 \Rightarrow \frac{120}{13} = V_x$$

$$V_x = 9.23 \quad \therefore i_1 = \frac{50 - 9.23}{10}$$

$$\Rightarrow \frac{40.77}{10} = 4.07 \approx 4A$$

Ans 27.

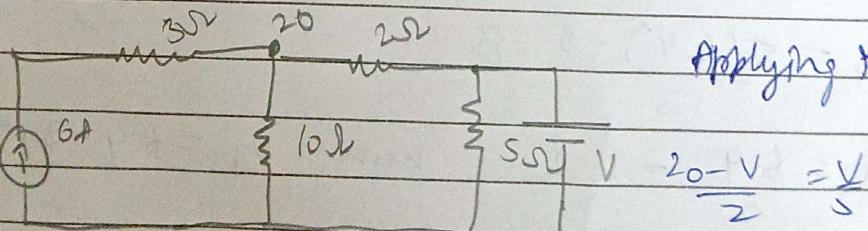

Applying KVL at node


$$\frac{20 - V}{2} = V$$

$$\Rightarrow 100 - 5V = 2V$$

$$150 = 7V$$

$$\therefore V = 14.28$$
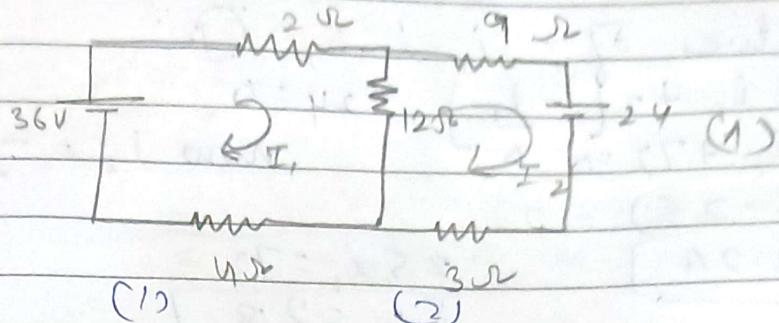
$$\therefore I \text{ through } 5\Omega = \frac{14.28}{8} = 1.85 \text{ A}$$



$$\text{In mesh 1} \rightarrow -2i_1 - i_2(i_1 - i_2) = 4i_1 + 36 = 0$$

$$\Rightarrow -2i_1 - i_2i_1 - 12i_2 - 4i_1 + 36 = 0$$

$$-18i_1 - 12i_2 + 36 = 0 \quad (1)$$

$$\text{mesh 2} \rightarrow -9i_2 - 24 - 3i_2 + 2(i_2 - i_1) = 0$$

$$-9i_2 - 3i_2 - 12i_2 + 12i_1 = 24 = 0$$


$$-24i_2 + 12i_1 = 24$$

$$-2i_2 + i_1 = 2 \quad \therefore i_1 = 2 + 2i_2$$

$$-18(2 + 2i_2) - 12i_2 + 36 = 0$$

$$-36 - 36i_2 - 12i_2 + 36 = 0$$
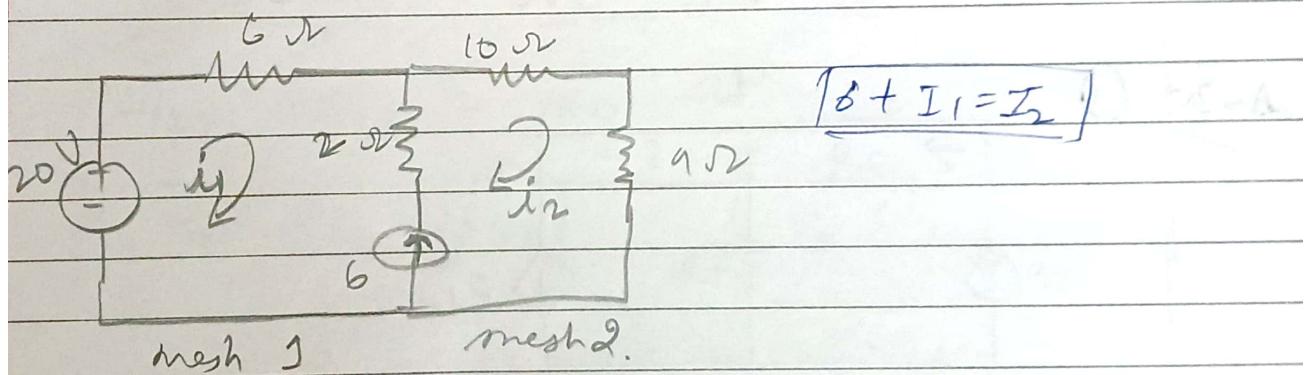
$$\boxed{i_2 = 0A} \quad \boxed{i_1 = 2A}$$



$$\text{for mesh 1:} \rightarrow -6i_1 - 2(i_1 - i_2) + 24 = 0$$

$$-6i_1 - 2i_1 + 2i_2 + 24 = 0$$

$$-8i_1 + 2i_2 + 24 = 0 \quad (1)$$

$$-6i_1 = -36 \quad \therefore i_1 =$$

$$\text{mesh 2:} -10i_2 - 4i_2 + 2(i_2 - i_1) = 0$$

$$-14i_2 + 2i_2 - 2i_1 = 0 \quad (2)$$

$$-12i_2 = 2i_1 \quad \therefore [i_1 = -6i_2]$$

Putting value of i_1 in eqn ①

$$\rightarrow -8i_1 + 2(-i_1) + 24 = 0$$

$$-24i_1 = i_1 + 72 \Rightarrow i_1 = \frac{72}{25} \quad \text{now } i_2 = -\frac{i_1}{6}$$


$$\begin{aligned} i_2 &= -(6 - 2.8) \\ &= [-3.2A] \end{aligned}$$

$$25i_1 = 72$$

$$[i_1 = 2.8]$$

Ans 28.

(*)

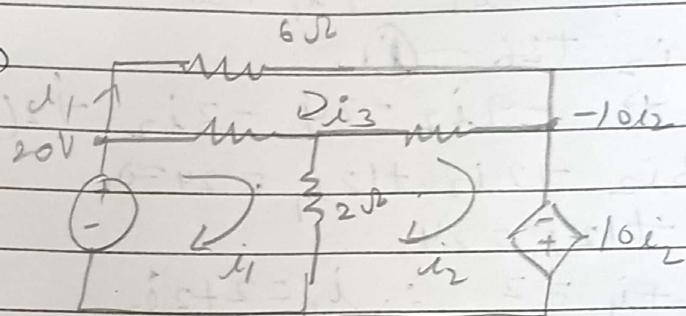

$$i_0 = \frac{20 + 10i_2}{6}$$


$$6i_0 - 10i_0 = 20$$

$$-4i_0 = 20$$


$$[i_0 = 5A]$$

Ans 30.

(1)

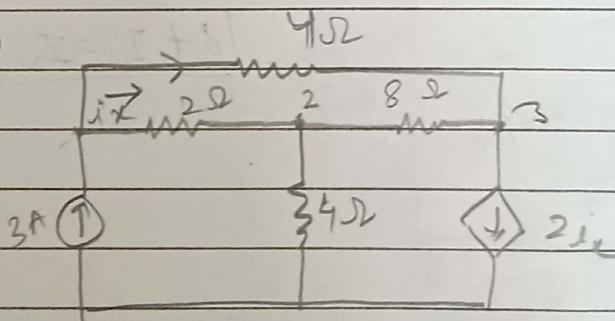

$$\text{At node } e_1 : 3 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4}$$

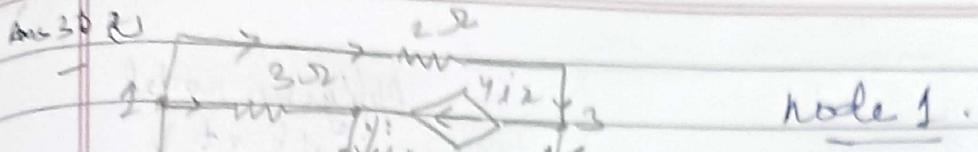

node 1.

$$\textcircled{1} \text{ PA: } 4V_1 - 4V_2 = I_1 \quad 10 = V_1 - V_2 + V_1 - \frac{V_3}{2}$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \textcircled{1}$$

$$\text{node } \textcircled{2} = \frac{V_1 - V_3}{2} - V_2 = \frac{V_3}{6}$$

node 2

$$\frac{V_1 - V_2}{3} - \frac{V_2}{4} - 4\left(\frac{V_2}{4}\right)$$

∴ L.R

$$\Rightarrow 4V_1 + 5V_2 = 0$$

$$\underline{\underline{4V_1 = V_2}} \quad \textcircled{2}$$

$$3V_1 - 4V_3 - 6V_2 = 0 \quad \textcircled{3}$$

$$(5V_1 - 3V_3 - 2V_2 - 60 = 0) \times 3$$

$$3V_1 - 4V_3 - 6V_2 = 0$$

$$3V_1 - 4V_3 - 6V_2$$

$$\underline{\underline{15V_1 - 9V_3 - 6V_2 = 180}}$$

$$-12V_1 + 5V_3 = -180$$

$$\boxed{V_3 = -180 + 12V_1}$$

Putting value of V_3 &
 V_3 in eq \textcircled{1}.


$$60 = 5V_1 - 2\left(-\frac{4V_1}{5}\right) - 3\left(-\frac{180 + 12V_1}{5}\right)$$

$$300 = 25V_1 + 8V_1 - 54V_1 + 540$$

$$\therefore \boxed{V_1 = 80}$$

$$\boxed{V_2 = -64}$$

$$\boxed{V_3 = 156}$$

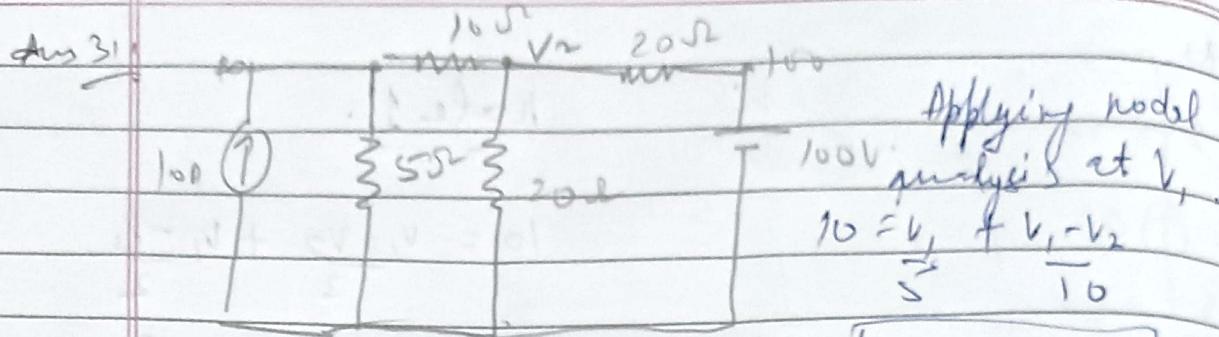

Applying nodal analysis at V_1 ,

$$10 = \frac{V_1 - V_2}{5} + \frac{V_1 - 100}{10}$$

$$100 = 2V_1 + V_2 - 100 \Rightarrow [3V_1 - V_2 = 200]$$

* nodal analysis at V_2 $[3V_1 - 100 = V_2]$

$$\frac{V_1 - V_2}{10} = \frac{V_2 - 100}{30} + \frac{V_2}{20}$$

$$6(V_1 - V_2) = 2(V_2 - 100) + 3V_2$$

$$\Rightarrow 6V_1 - 6V_2 = 2V_2 - 200 + 3V_2$$

$$6V_1 - 6V_2 = 5V_2 - 200$$

$$6V_1 + 200 = 11V_2$$

$$6V_1 + 200 = 11(3V_1 - 100)$$

$$6V_1 + 200 = 33V_1 - 1100$$

$$1300 = 27V_1$$


$$V_1 = 48.14$$

$$V_2 = 44.42$$

$$\therefore I_1 = \frac{V_1 - V_2}{10} = \frac{48.14 - 44.42}{10} = 0.372$$

$$I_2 = \frac{V_2 - 100}{30} = \frac{44.42 - 100}{30} = -1.85 A$$

Ans 32.

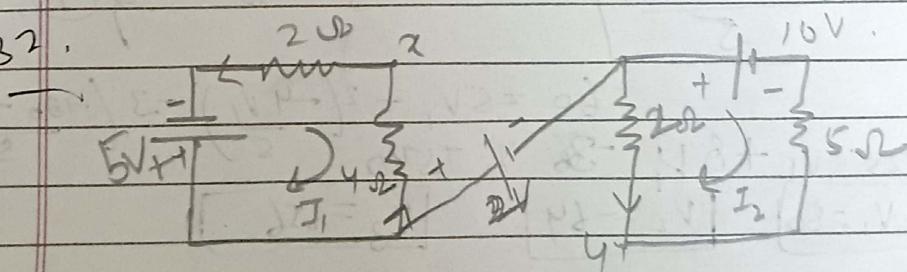

$$\text{for } I_1 = \frac{5}{2+4} = \frac{5}{6} = 0.833 A$$

$$T_2 = \frac{10}{7} \approx 1.428 \text{ A.}$$

Now voltage drop across $x \& y$.

$$V_x + 4x 5.83 - 2 - 2x 1.48 = V_y$$


($+V_c$ as we are crossing the resistances
in opp. dirn of current)

$$V_x + 3.32 - 2 - 2.96 = V_y$$

$$V_x = 3.32 - 4.96 = V_y$$

$$V_x - V_y = 1.64 \rightarrow \text{P.drop.}$$

Ans 33.

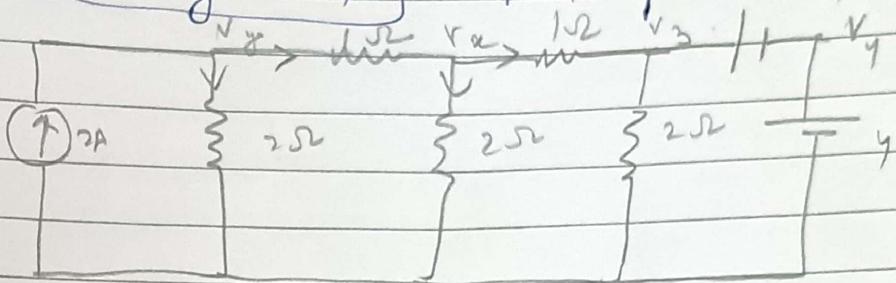

$$\text{At } V_y \Rightarrow 2 = \frac{V_y}{2} + \frac{V_y - V_x}{1}$$

$$4 = 3V_y - 2V_x \quad \textcircled{1}$$

$$\text{at } V_x \Rightarrow V_y - V_x = V_x + \frac{2}{1} + \frac{V_x}{2}$$

$$= 2V_y - 5V_x + 4 = 0 \quad \textcircled{2}$$

$$\frac{4 - 3V_y}{-2} = V_x$$

$$\rightarrow 2V_y - 5 \left(\frac{4 - 3V_y}{2} \right) + 4 = 0$$

$$2V_y + 5 \left(\frac{4 - 3V_y}{2} \right) + 4 = 0$$

$$2V_y + 20 - 15V_y + 4 = 0$$

$$4V_y + 20 - 15V_y + 8 = 0$$

$$+ 11V_y = + 28$$

$$\therefore V_y = 2.54$$

$$\boxed{V_y = 2.54}$$

$$\therefore V_x = 4 - 3V_y = 1.81$$

$$\frac{4 - 7.62}{-2} = V_x$$

$$\therefore \boxed{V_x = 1.81}$$

$$\therefore V_1 = 2.54, V_2 = 1.81$$

$$V_3 = 2$$

$$V_y = 4 - 2 = \boxed{2V}$$